


Robert Bara Assignment 1-Boost Converter Analysis

Friday, January 28, 2022

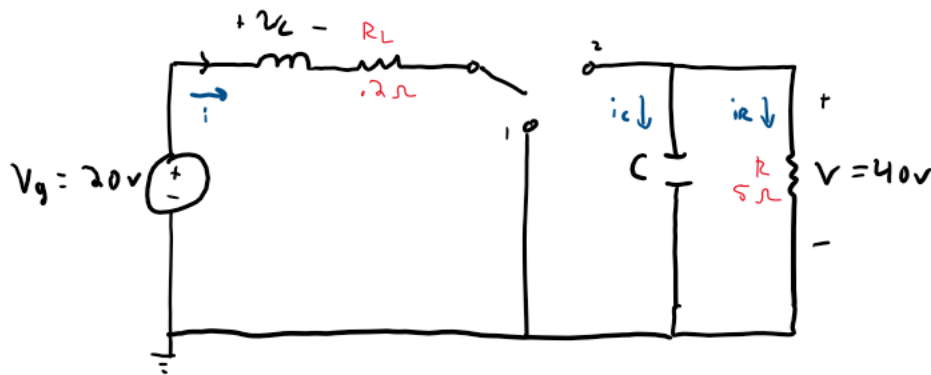10:43 AM

Assignment #1

- Assignment #1: For the boost converter shown below (considering losses at inductor resistance),
- 1) If $f_s = 10 \text{ kHz}$, $V = 40 \text{ V}$, $V_g = 20 \text{ V}$, $R = 5 \Omega$, $R_L = 0.2 \Omega$ (inductor resistance), $D < 80\%$, please draw the waveforms of v_L and i_C (voltage and current ripples are not considered, the values of v_L and i_C should be shown in the waveforms).



Find The Period from the Sample frequency

$$T_s = \frac{1}{f_s} = \frac{1}{10e^3} = 0.001 \text{ sec}$$

Find D from Voltages $V = M(D)V_g$


$$M = \frac{V}{V_g} = \frac{40}{20} = 2 \quad M = \frac{1}{1-D} \text{ for Boost Converter}$$

$$M = \frac{1}{1-D} \Rightarrow 2 = \frac{1}{1-D} \Rightarrow 1-D = \frac{1}{2} \Rightarrow -D = \frac{1}{2} - 1 \Rightarrow D = 1 - \frac{1}{2}$$

$$\Rightarrow \boxed{D = \frac{1}{2}}$$

$$\boxed{D' = 1-D = 1 - \frac{1}{2}}$$

Position 1:

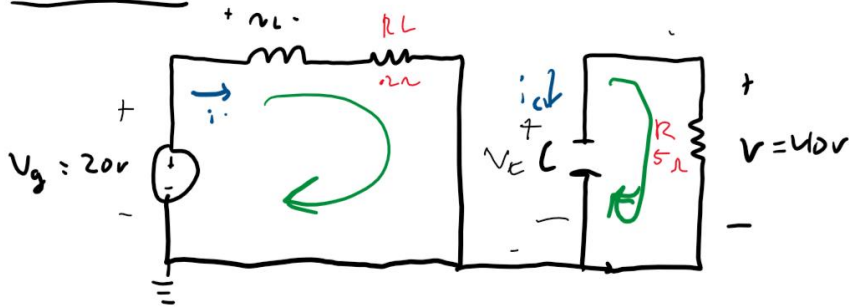

$$V = IR$$

KVL: $-V_g + v_L(t) + v_{RL}(t) = 0$

$$v_L(t) = V_g - i_L(t)R_L$$

Small Ripple approximation: $v_L(t) \approx V$; $i_L(t) \approx I$
 $i_L(t) \approx I_L$

$$V_L = V_g - I R_L$$

$$V_L = 20 - I R_L$$

$$V_L = 20 - I(2\Omega)$$

$$I_0 = \frac{V}{R} = \frac{40V}{5\Omega} = 8A$$

$$V = M(D)V_g$$

$$I_g = M(D)I$$

Finding I since $M(D) = 2$;


$$I = (2)(8A) = 16A$$

KCL: $I_L = I - I_D = 16A - 8A = 8A$

$$\therefore V_L = 20 - (16A)(2\Omega)$$

$$V_L = 16.8V$$

Position 2:

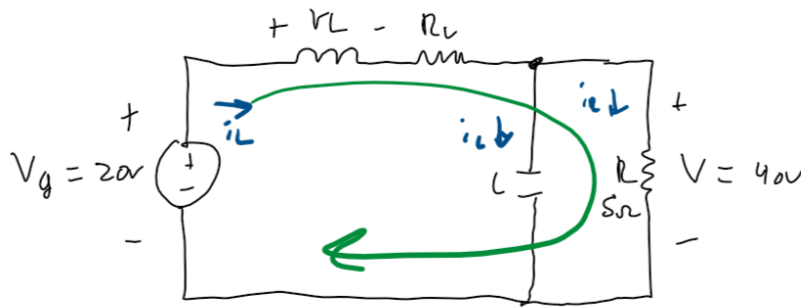

$$KVL: -V_g + v_L(t) + v_R(t) + V = 0$$

Small ripple approximation

$$\Rightarrow V_L = V_g - V_{RL} - V \Rightarrow V_L = V_g - I_{RL} - V$$

Small ripple approx: $I_c = I - \frac{V}{R} \Rightarrow I_c = I - \frac{40V}{8\Omega} = I - 8A$

$$0 = \langle v_L(t) \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = D(V_g - I_{RL}) + D'(V_g - I_{RL} - V)$$

$$\Rightarrow D(V_g - I_{RL}) + (1-D)(V_g - I_{RL} - V)$$

$$0 \Rightarrow V_g - I_{RL} - D'V$$

$$0 = \langle i_L(t) \rangle = D\left(-\frac{V}{R}\right) + D'\left(I - \frac{V}{R}\right)$$

$$\Rightarrow D\left(-\frac{V}{R}\right) + (1-D)\left(I - \frac{V}{R}\right)$$

$$0 \Rightarrow D'I - \frac{V}{R}$$

$$\rightarrow D'I - \frac{V}{R} = V_g - I_{RL} - D'V$$

plug in values: $\frac{1}{2}I - 8A = 20V - 0.2I - \frac{1}{2}(40V)$

$$0.5I - 8A = \cancel{20V} - 0.2I - \cancel{20V}$$

$$.5I - 8A = -.2I$$

$$.7I = 8A$$

$$I = 11.43A$$

$$\therefore V_L = V_g - I_{RL} - V$$

$$= 20 - (11.43)(6.25) - 40$$

$$V_L = -22.29V$$

$$\therefore I_c = I - \frac{V}{R}$$


$$I_c = 11.43 - 8A$$

$$I_c = 3.43A$$



Find the period of the signal

$$\delta T_s = \frac{1}{2} \left(\frac{1}{0.001} \right) = 500$$
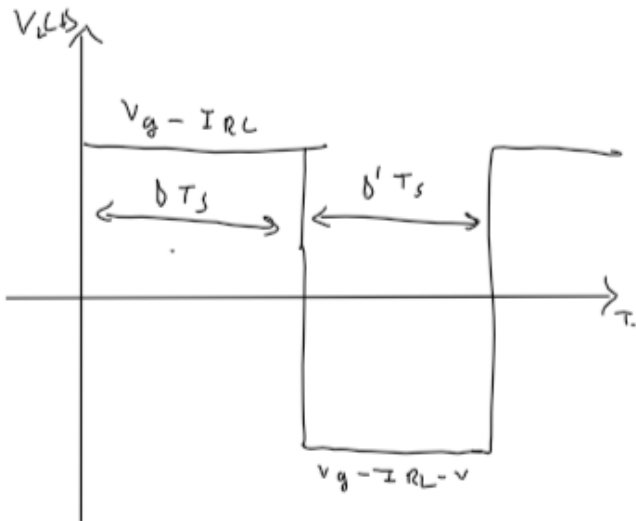
$$\delta' T_s = \left(1 - \frac{1}{2} \right) \left(\frac{1}{0.001} \right) = 500$$



Plug in
equations/values
 \Rightarrow

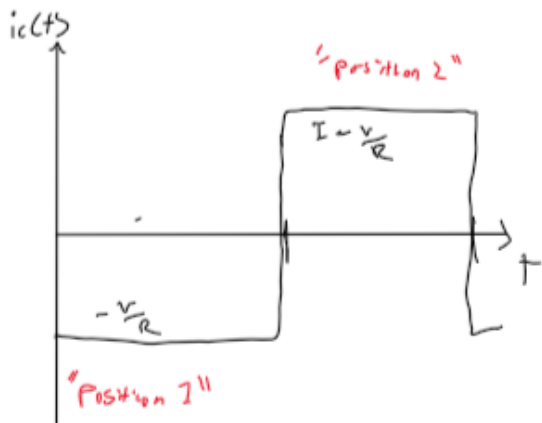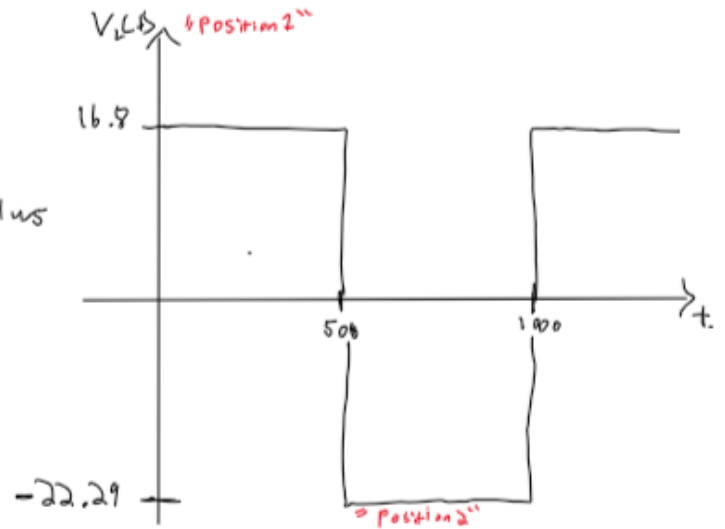

plug in
values
 \Rightarrow

