

Lab 7. DC Models for Bipolar Transistors

In this lab, you will be looking at some of the crucial applications of transistors in the real world, why they are important, why we use them, and what they can do. A transistor, similar to a faucet, can control the flow of electrical current.

In this lab, you will look at the definition and the importance of a transistor and observe the patterns of behavior of a bipolar junction transistor (BJT) using several different methods.

Learning Objectives

After completing this lab, you will be able to complete the following activities:

1. Determine if the transistor is PNP or NPN;
2. Identify the base, collector, and emitter leads;
3. Measure the reverse breakdown voltage for the base-emitter junction;
4. Construct and use a circuit to plot the I_C vs. V_{CE} for different values of I_B ;
5. Construct and use a circuit to plot I_B vs. V_{BE} .
6. Determine β_{DC} , I_{CEO} , R_{BB} , and V_0 and draw and label a DC model for a transistor.

Required Tools and Technology

Platform: NI ELVIS II/II+

Instruments used in this lab:

- Instrument 1: Function Generator
- Instrument 2: Oscilloscope
- Instrument 3: Variable Power Supply

Note: The NI ELVIS Cables and Accessories Kit (purchased separately) is required for using the instruments.

View User Manual:

<https://bit.ly/36DFFrv>

<https://bit.ly/36CnQZH> (Credit to Clemson University)

View Tutorials:

<https://bit.ly/35Ae9Kc> (Credit to Colorado State University)

Install Soft Front Panel support:

<https://bit.ly/2NbhTv6>

Hardware: NI ELVIS II/II+ Default Prototyping Board

View Breadboard Tutorial:

<http://www.ni.com/tutorial/54749/en>

Hardware: Electronics Kit

- Various values of resistors
- BJT, 2N3904 or similar

Software: NI Multisim Live

Access online <http://multisim.com>

View Help <http://multisim.com/help/>

1. Background Information

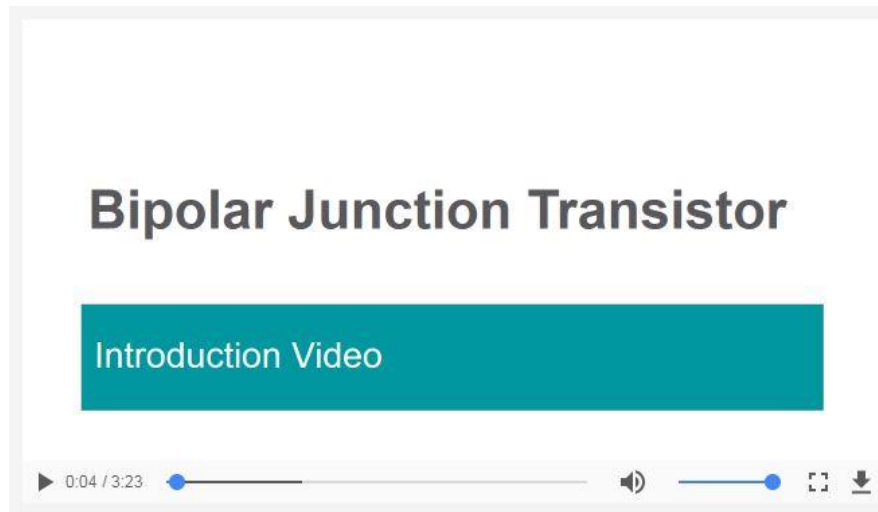


Figure 1. Video Screenshot. View the video here: youtu.be/YCD7nszsfFM

Video Summary

- A transistor controls the flow of electrical current.
- Transistors have two common applications: as switches, and as amplifiers.
- When you switch between the cut-off and saturation regions of a circuit, it is the same as the differences between an open and closed circuit.

1.1. What is a BJT?

A bipolar junction transistor (BJT) is a device with three terminals capable of amplifying a signal. A BJT is made up of three layers of N-type and P-type doped semi-conducting material. The terminals are known as base (B), collector (C) and emitter (E).

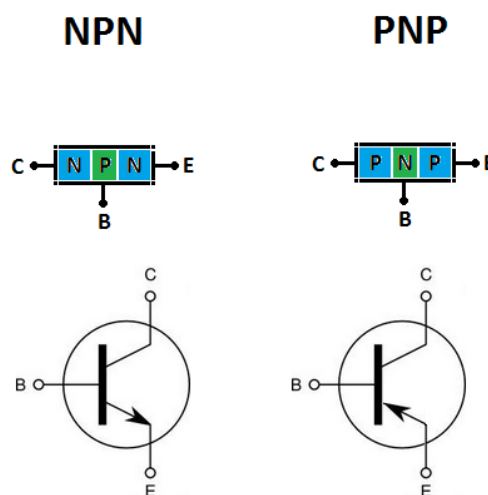


Figure 2. NPN and PNP transistors

A small current at the base is amplified to a larger current in a collector-emitter circuit.

An important feature is the current gain under direct current, beta (β_{DC}), which is the relationship between the current at the collector and that at the base. Another parameter is beta under alternate current (β_{AC}), which is the change in collector current divided by the change in base current.

1.3. What Do Transistors Do?

A transistor is similar to a faucet. As you know, a faucet controls water flow. A faucet can start, stop, and adjust flow. A transistor controls the flow of electrical current in much the same way.

1.4. Why Are Transistors Important?

Small, modern devices and mobile phones require transistors. Before the invention of transistors, electronic devices required large vacuum tubes.

Vacuum tubes were big, fragile, cumbersome, and hard to keep cool. With the invention of transistors, electronics became smaller and cheaper, allowing for more extensive access to them. Extensive access to electronics has shaped our society for the last 60 years. All of this was made possible because of the use of transistors in electronic devices.

1.5. BJT design

As the name suggests, a bipolar junction transistor functions by leveraging the flow of both negatively charged electrons and the positively charged *holes* in a doped semiconductor. A BJT is formed by placing two PN junctions together with opposite polarities, either PNP or NPN. Normally, this would simply act as an open circuit, since one or the other of the PN junctions would be strongly reverse biased. However when positive or negative current is injected into the middle layer of this semiconductor sandwich, the bias voltage across both junctions can be adjusted so as to control current flow from the emitter to the collector.

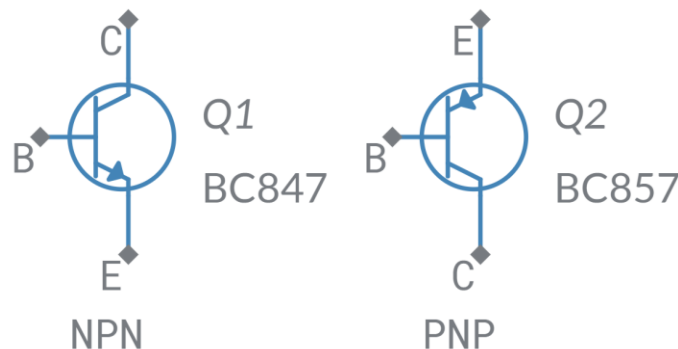


Figure 3. BJT schematic symbols with labelled terminals

Whereas with a field effect transistor we were interested in the gate voltage, with a junction transistor we are concerned with the current flow from the base to the emitter. This flow of current changes the charge distribution in the depletion region of the PN junctions of the transistor allowing for control of the total resistance across emitter to collector.

1.6. BJT operation

The operating mode of a BJT is determined by the bias state of the emitter-base and collector-base PN junctions. The modes are listed in table 1.

Table 1. BJT Operation mode

Mode	E-B junction bias	C-B junction bias
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

In the cutoff mode, both junctions are reverse biased and no current flows (excepting the very small reverse current of the PN junctions). Conversely when both junctions are forward biased in saturation mode, current can flow freely. These states correspond to the “off” and “on” states when a transistor is being used as a switch. Between these two extremes is the active mode, where only the emitter-base junction is forward biased, and the current flow from emitter to collector can be significantly changed using minor variations in the base current.

1.7. DC Models for Bipolar Transistors

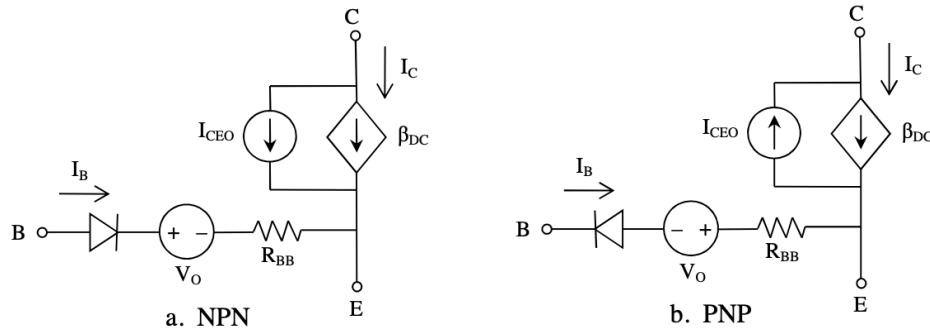


Figure 4. DC Models showing the base-emitter diodes

The models shown in Figure 4 include base-emitter diodes. These diodes indicate that current must flow into the base of the NPN and out of the base of the PNP. For the NPN, no base current will flow until V_{BE} is greater than V_O . For the PNP, no base current will flow until V_{BE} is less than V_O . Since these DC models are used for operating point design calculations, it is assumed that the base currents will have the correct polarity; therefore, the base-emitter diodes need not be shown.

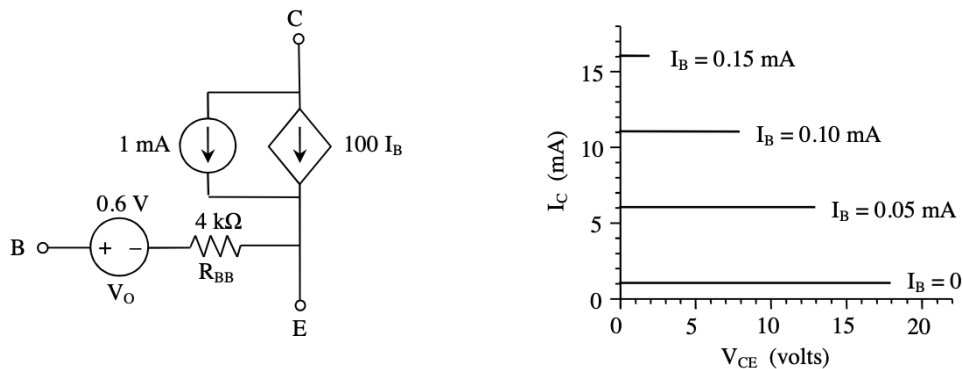


Figure 5. (Left) DC model for an NPN transistor, $\beta_{DC} = 100$, (Right) Collector characteristics for the DC model

Figure 5 (Left) shows a model for a particular transistor. The curves shown in Figure 5 (Right) are the *collector characteristics* of the transistor. Each curve (horizontal line segment) is the IV characteristic of the collector-emitter terminals for a constant base current. β_{DC} and I_{CEO} may be determined from the collector characteristics (and vice-versa):

I_{CEO} is the collector current that flows when $I_B = 0$. $I_{CEO} = 1 \text{ mA}$. (Exaggerated for illustration)

From the model: $I_C = \beta_{DC} I_B + I_{CEO}$. Therefore, $\beta_{DC} = (I_C - I_{CEO}) / I_B$. $\beta_{DC} = 100$. V_O and R_{BB} are determined from the input curve (I_B vs. V_{BE}).

2. Exercises

2.1. Simulation of NPN

Multisim includes a tool to sweep through different voltage values and measure different output parameters called DC Sweep Analysis.

Build the following circuit in multisim

Use any NPN BJT (Found under the Transistor tab → NPN BJT)

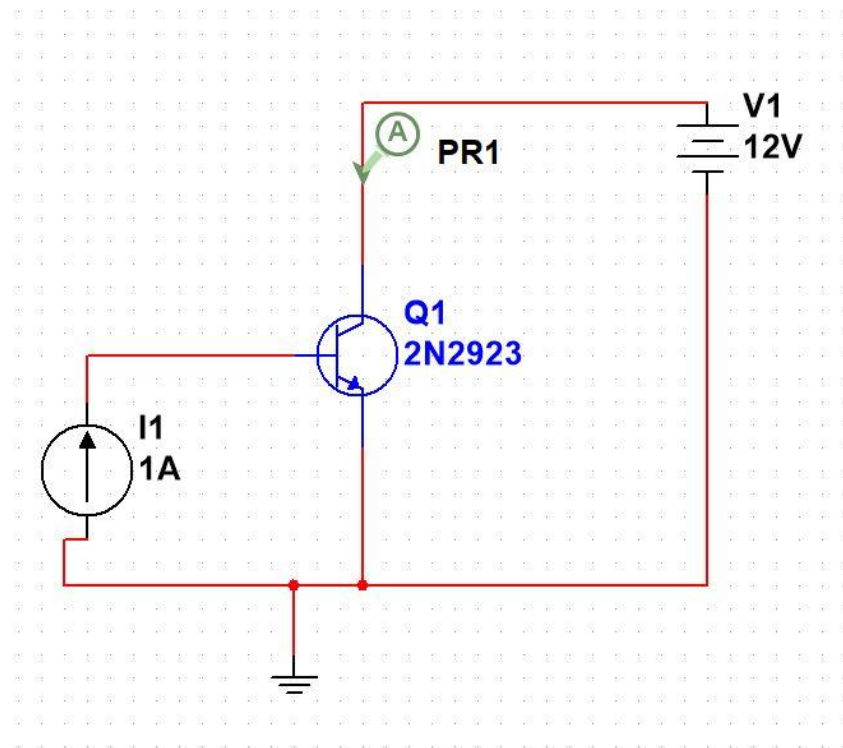


Figure 6: NPN circuit

1. Select Simulate → Analyses → DC sweep from the shortcut menu to open this tool.
2. DC Sweep Analysis → Analysis parameters
3. Source 1 determines which variable will be graphed along the X axis. We want to show Collector voltage, so set Source to VC.

4. Set Start value to 0 V.
5. Set Stop value to 1 V
6. Set Increment to 0.005V.
7. Enable the Use source 2 checkbox.
8. Source 2 determines which variable will be used to create multiple plots. We want to create plots of Base current, so set Source to IB.
9. Set Start value to 0.00015A. (this is .15mA)
10. Set Stop value to 0.0006A. (this is .6mA)
11. Set Increment to 0.0001125A. (this is .1125mA)

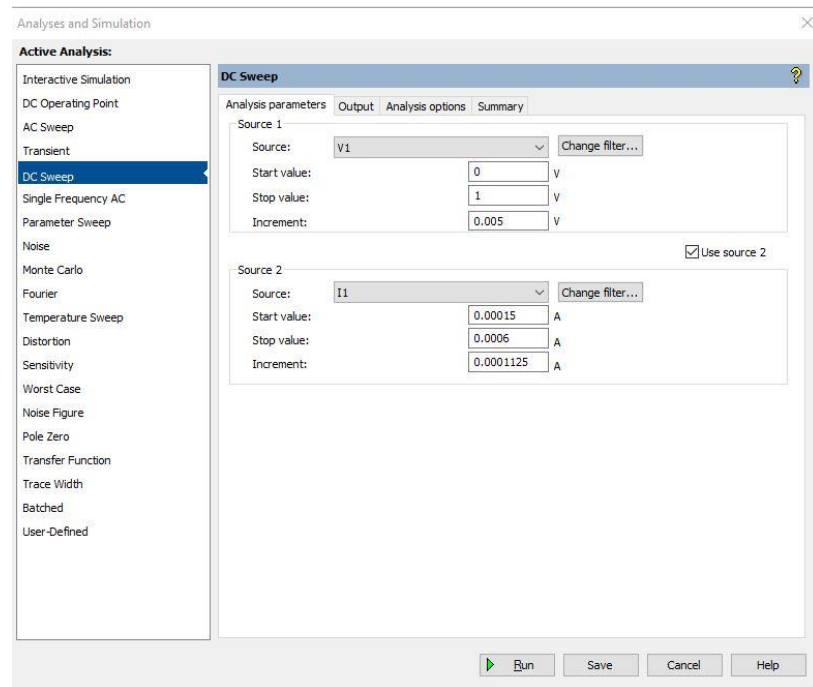


Figure 7 DC Sweep Settings

Running the Simulated Sweep

1. Select the Output tab.
2. We want the Base current to be graphed along the Y axis, so select I(Q1[IC]) from the variables list, and click Add.
3. Click the Simulate button to run the simulated sweep.

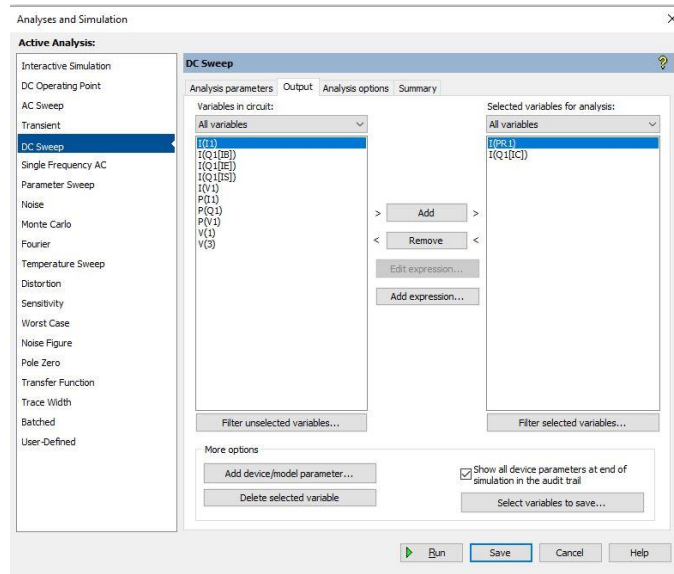


Figure 8 DC Sweep Output settings

Q.1) At what approximate Voltage value do the different plots start separating from each other?

2.2. Simulation: PNP Transistor

Construct the following circuit in multisim:

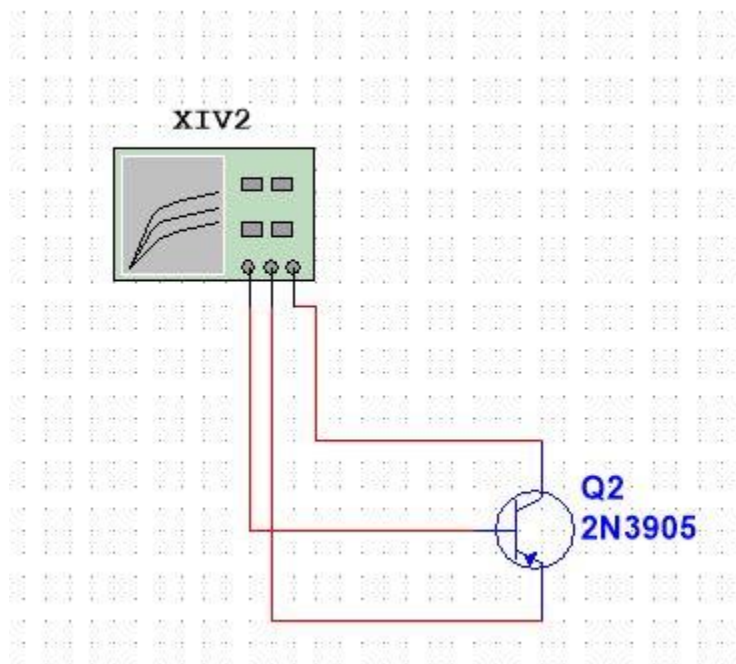


Figure 9 PNP Circuit

The IV Analyzer can be found under Simulate → instruments → IV Analyzer

For this any PNP BJT can be used (found under the transistor tab → PNP BJT category)

1. Double click the IV Analyzer
2. Set the component to BJT PNP (red box)
3. Select Simulate Parameter (Blue box)
4. Set the V_{ce} column as follows
 - a. Start 0 V
 - b. Stop 1 V
 - c. Increment 50 mV
5. Set the I_b column as follows
 - a. Start 1 mA
 - b. Stop 10mA
 - c. Num Steps 5

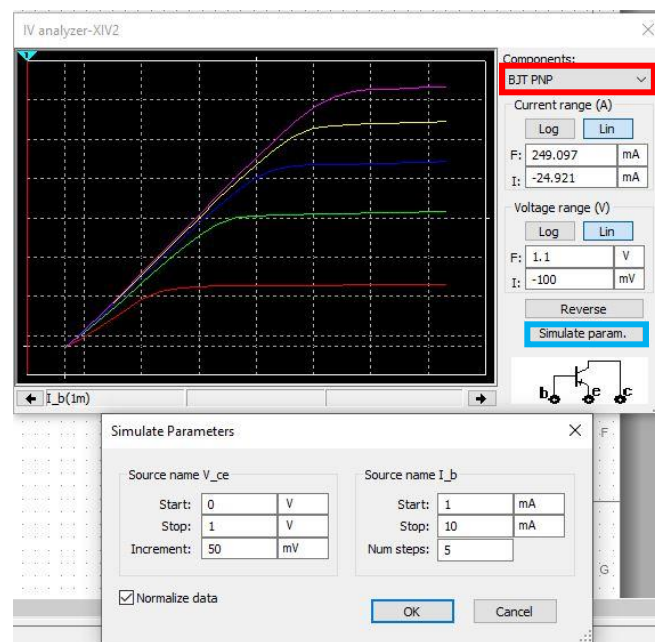


Figure 10 IV Analyzer Settings

Analyze the Results

Analyze the results. The graph shows 5 curves, each corresponding to the relationship between the Collector Emitter Voltage (V_{CE}) and the Collector Current (I_C) for different Base Currents (I_B).

Note: The five curves correspond to Base Currents of 1 through 10 mA. These plots represent the increasing current flowing through the transistor as the voltage increases at the Collector.

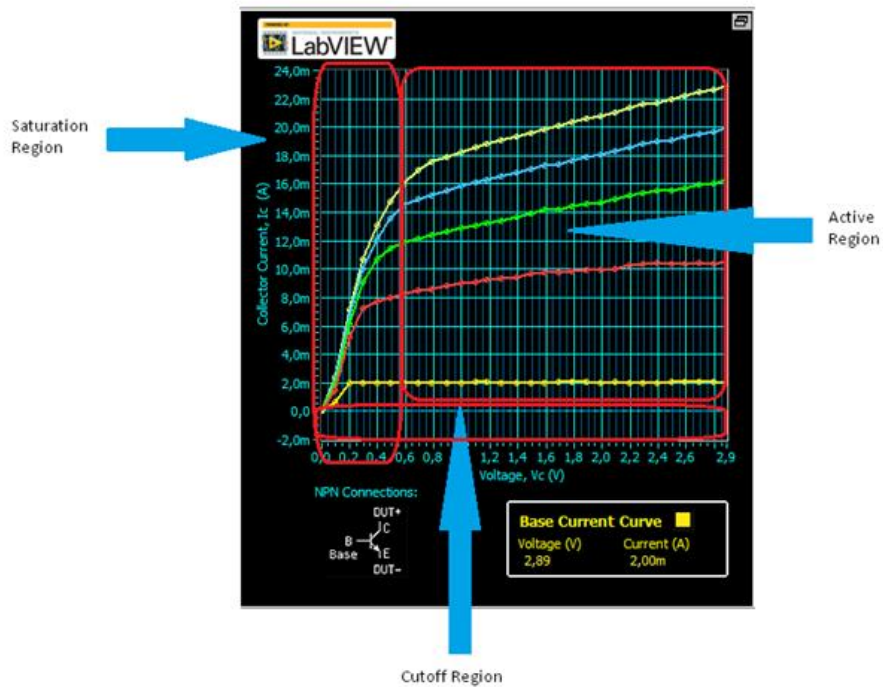


Figure 11: IV Curve generated from hardware

Using these characteristic curves, we can define 3 transistor regions of operation:

- **Cutoff region:** In this region, the transistor does not conduct current from the collector to the emitter (open interrupter).
- **Saturation region:** The transistor has a maximum V_{CE} known as $V_{CE\text{ sat}}$. When V_{CE} drops below $V_{CE\text{ sat}}$, the transistor will conduct the maximum possible I_{max} current, given the actual base current defined by the circuit's polarization. In practical terms, when the transistor operates under saturation, it will behave almost like a cable (closed interrupter).
- **Active region:** In this region, the collector current I_C behaves like a linear function of the base current defined by the β constant (depending on the type of transistor).

$$I_C = \beta I_B$$

For practical purposes, if we need the transistor to act like an interrupter, we will work in the cutoff and saturation regions. If on the other hand we need to use the transistor as an amplifier, we need to work in the active region.

These questions will help you review and interpret the concepts learned in this lab.

Q.2) How does this voltage (From Q1) compare to the graph recorded when simulating the circuit previously (the NPN vs the PNP) ?

Q.3) Does this voltage correspond to the point on the graph when current began to flow? Explain.

APPENDIX

The following is the template of the ECE 3313 report. Note that the report must be typed using Microsoft Words/Excel. Please download the template from the Canvas website.

ECE 3313 Lab X Report	Your Name
<u>Title:</u> Lab 1: Observation, Modeling, and Communication	
NAME:	Partner:
General Objective: One or two sentences that describe the objective of this specific lab.	
1.0 Prelab Activities: If there is any	
2.0 Background Activities: Read background information and summarize important theory, equation, etc.	
3.0 Procedure: Describe step-by-step procedure, including circuit schematic, calculation, and etc.	
4.0 Results: A lab often includes questions. Please include your answer under the result sections. 4.1 Simulation Results: Make sure to fully discuss about the results, figure, etc. 4.2 Experimental Results: Make sure to fully discuss about the results, figure, etc.	
5.0 Conclusions	

Remark: Your lab report should include ALL relevant calculations, pictures and work needed for completion of the experiment. Circuit output validation using Multisim is also required. Detailed explanations for decisions made throughout the lab need to be included in the Discussion section of your report as outlined in the Report Guidelines.

Disclaimer: Some of this lab contents includes portion of National Instruments' published resources in their website (NI.com). The permission is obtained from the National Instruments.

© 2018 National Instruments

All rights reserved. Neither this resource, nor any portion of it, may be copied or reproduced in any form or by any means without written permission of the publisher.

National Instruments respects the intellectual property of others, and we ask our readers to do the same. This resource is protected by copyright and other intellectual property laws. Where the software referred to in this resource may be used to reproduce software or other materials belonging to others, you should use such software only to reproduce materials that you may reproduce in accordance with the terms of any applicable license or other legal restriction.

LabVIEW and National Instruments are trademarks of National Instruments.

All other trademarks or product names are the property of their respective owners.

Additional Disclaimers: The reader assumes all risk of use of this resource and of all information, theories, and programs contained or described in it. This resource may contain technical inaccuracies, typographical errors, other errors and omissions, and out-of-date information. Neither the author nor the publisher assumes any responsibility or liability for any errors or omissions of any kind, to update any information, or for any infringement of any patent or other intellectual property right.

Neither the author nor the publisher makes any warranties of any kind, including without limitation any warranty as to the sufficiency of the resource or of any information, theories, or programs contained or described in it, and any warranty that use of any information, theories, or programs contained or described in the resource will not infringe any patent or other intellectual property right. THIS RESOURCE IS PROVIDED "AS IS." ALL WARRANTIES, EITHER EXPRESS OR IMPLIED, INCLUDING, BUT NOT LIMITED TO, ANY AND ALL IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS, ARE DISCLAIMED.

No right or license is granted by publisher or author under any patent or other intellectual property right, expressly, or by implication or estoppel.

IN NO EVENT SHALL THE PUBLISHER OR THE AUTHOR BE LIABLE FOR ANY DIRECT, INDIRECT, SPECIAL, INCIDENTAL, COVER, ECONOMIC, OR CONSEQUENTIAL DAMAGES ARISING OUT OF THIS RESOURCE OR ANY INFORMATION, THEORIES, OR PROGRAMS CONTAINED OR DESCRIBED IN IT, EVEN IF ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, AND EVEN IF CAUSED OR CONTRIBUTED TO BY THE NEGLIGENCE OF THE PUBLISHER, THE AUTHOR, OR OTHERS. Applicable law may not allow the exclusion or limitation of incidental or consequential damages, so the above limitation or exclusion may not apply to you.